

ADVANCED DIGITAL DESIGN: EXPERIMENT #6

GENERIC MULTIPLIER/MAC

Purpose

The purpose of this experiment is to write a generic 2^s Complement multiply and accumulate (MAC) unit (for grad students) or multiplier (for undergrads).

References

1) ModelSim Tutorial: from ModelSim, click on Help->PDF Documentation->Tutorial

Problem: Design a Generic Structural Synchronous 2^s Complement MAC (for grad students)

- * entity name: *MAC*
- * generic constants: *X_len*, *Y_len*: positive, default to 4 ($X_len \leq Y_len$); *A_len*: positive, default to 8
- * inputs: *X*, *Y*: arbitrary length std_logic_vector (assume ≥ 4); *reset*, *clk*: std_logic
- * outputs: *A*: arbitrary length std_logic_vector (assume $\geq X_len + Y_len$); *OV*: std_logic

- * name your file: MAC.vhd
- * include as comments: name and student number (-- precedes a comment line)
- * use the array structured multiplication algorithm
- * since this is a structural design, only port mapping of components is allowed (e.g., no processes, dataflow equations, functions, procedures, etc.)

- * email your main design, components, and testbench(es) to the TA: mousam.hossain@ndsu.edu
- * your design will then be run on my testbenches
- * make sure that all names and input/output order match those on this sheet, otherwise your design will not run on my testbenches and points will be deducted

- * Turn in a report including the following: **130 total points**
 - project description
 - Block Diagram of MAC Chip
 - gate-level design of MAC components (i.e., FA, HA, AND2, NAND2, OV, DFF0, etc.)
 - component level diagram of the following sized MACs
 - > 8+4×4
 - > 12+5×4
 - MAC VHDL code
 - VHDL testbench(es), testing 8+4×4 and 12+5×4 MACs

Hints:

- inputs needed to generate OV are: the sign bits of X, Y, Aold, and Anew ($Anew = Aold + X * Y$)
- the following constructs may be helpful:
 - type twoD_array is array(3 downto 0, 3 downto 0) of std_logic;
 - signal intermediate: twoD_array;
 - intermediate(3, 0) <= D; -- D is defined as std_logic

Problem: Design a Generic Structural Boolean 2^s Complement Multiplier (for undergrads)

- * entity name: *MULT*
- * generic constants: *X_len*, *Y_len*: positive, default to 4 ($X_len \leq Y_len$)
- * inputs: *X*, *Y*: arbitrary length std_logic_vector (assume ≥ 4);
- * outputs: *P*: std_logic_vector of length $X_len + Y_len$;

- * name your file: MULT.vhd
- * include as comments: name and student number (-- precedes a comment line)
- * use the array structured multiplication algorithm

- * email your main design, components, and testbench(es) to the TA: mousam.hossain@ndsu.edu
- * your design will then be run on my testbenches
- * make sure that all names and input/output order match those on this sheet, otherwise your design will not run on my testbenches and points will be deducted

- * Turn in a report including the following: **130 total points**
 - project description
 - Block Diagram of MULT Chip
 - gate-level design of MULT components (i.e., FA, HA, AND2, NAND2, etc.)
 - component level diagram of the following sized Multipliers
 - > 4×4
 - > 5×4
 - MULT VHDL code
 - VHDL testbench(es), testing 4×4 and 5×4 Multipliers

Hints:

- the following constructs may be helpful:
 - type twoD_array is array(3 downto 0, 3 downto 0) of std_logic;
 - signal intermediate: twoD_array;
 - intermediate(3, 0) <= D; -- D is defined as std_logic

- * **reports and emailed code due Friday, May 3, but will not be considered late until Tuesday, May 7 at 5:00 pm**